

第十章 含有耦合电感的电路

主要内容:


1、互感

2、含有耦合电感电路的分析计算

3、理想变压器

§ 10-1 互感

一、磁耦合

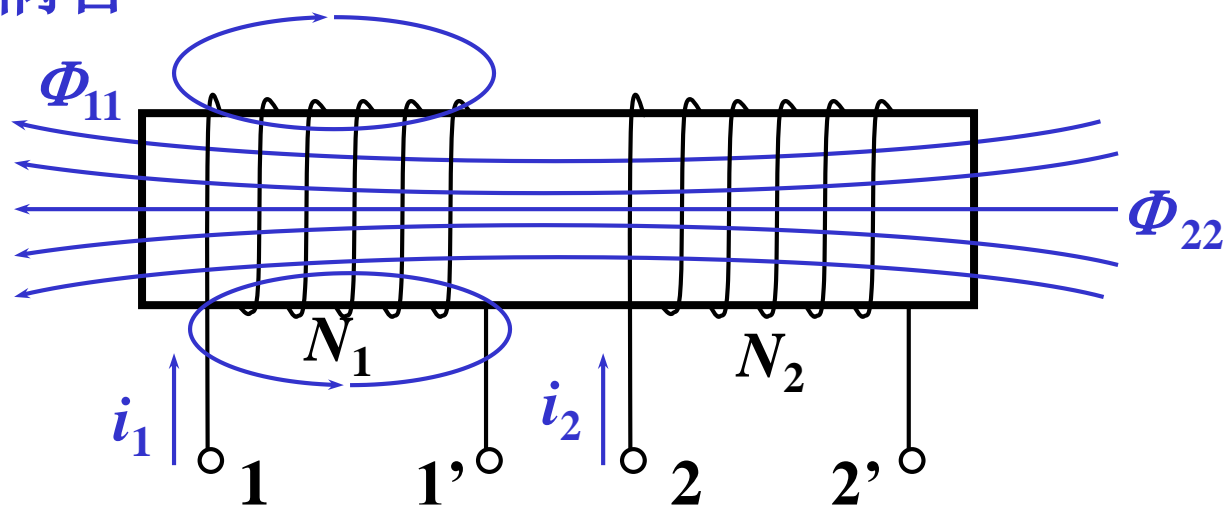

施感电流 i_1 \longrightarrow Φ_{11}

Φ_{11} splits into two paths:

- ψ_{11} (self-flux)
- ψ_{21} (mutual flux)

施感电流 i_2 \longrightarrow Φ_{22}

Φ_{22} splits into two paths:

- ψ_{22} (self-flux)
- ψ_{12} (mutual flux)

二、两个线圈耦合时的磁通链

自感磁通链₁

$$\psi_{11} = L_1 i_1$$

$$\psi_{22} = L_2 i_2$$

互感磁通链₁

$$\psi_{12} = M_{12} i_2$$

$$\psi_{21} = M_{21} i_1$$


线圈1中的磁通链₁

$$\Psi_1 = \Psi_{11} + \Psi_{12} = L_1 i_1 \pm M_{12} i_2$$

线圈2中的磁通链₁


$$\Psi_2 = \Psi_{22} + \Psi_{21} = L_2 i_2 \pm M_{21} i_1$$

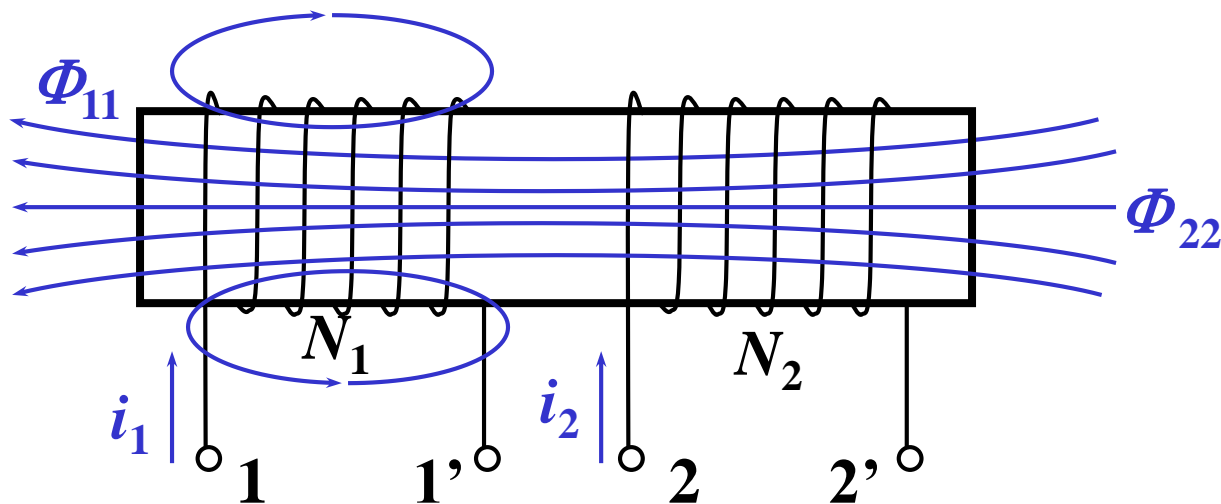同名端：当两个电流分别从两个线圈的对应端子流入，其所产生的磁场相互加强时，则这两个对应端子称为同名端。




确定同名端的方法:

(1) 使用右手螺旋法则，根据线圈的绕向和相对位置来判断。

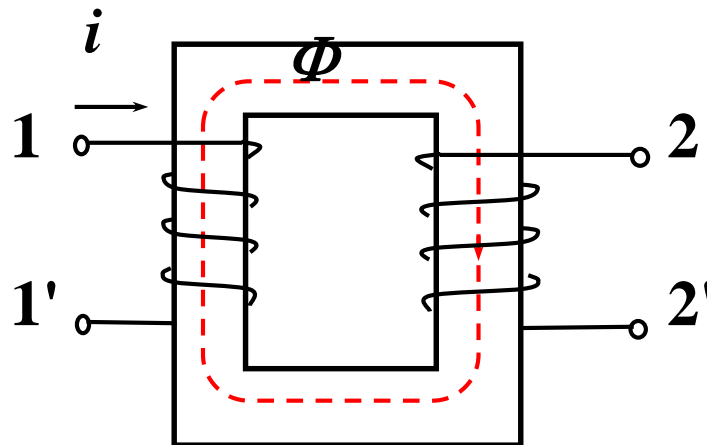

(2) 用实验的方法来判断。

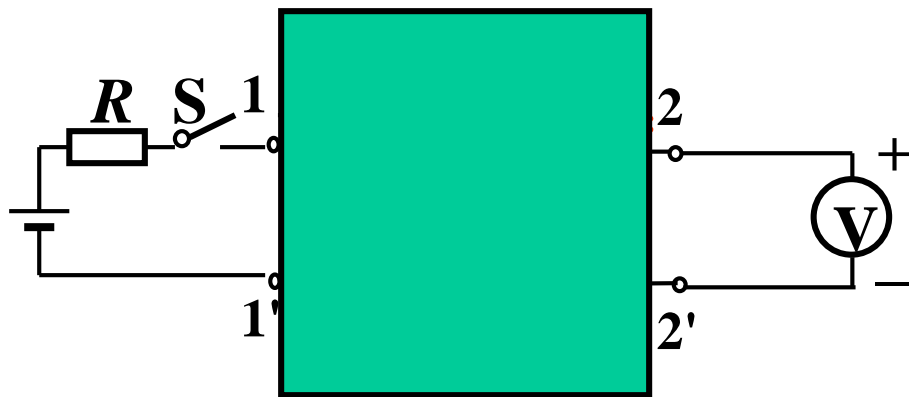


如图电路，当闭合开关S时， i 增加，

$$\frac{di}{dt} > 0, \quad u_{22'} = M \frac{di}{dt} > 0 \quad \text{电压表正偏。}$$

多个线圈耦合的情况


$$\psi_k = \psi_{kk} + \sum_{j \neq k} \psi_{kj}$$

ψ_{kj} 与 ψ_{kk} 同向取“+”，反之取“-”。

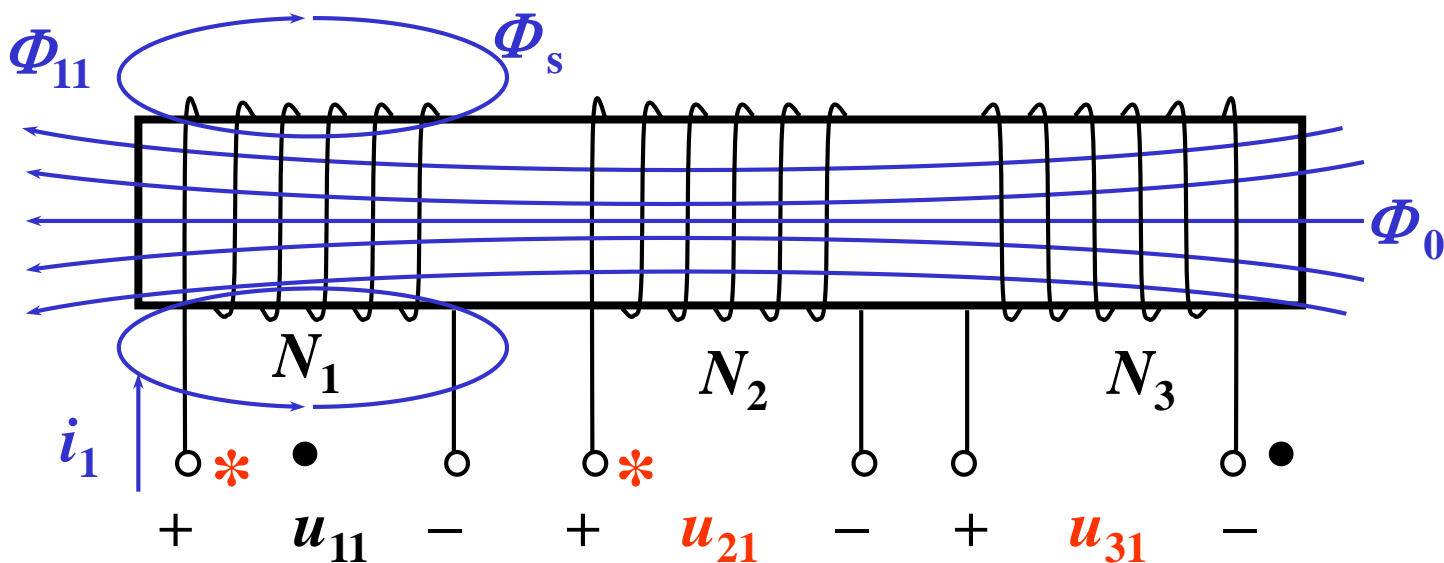

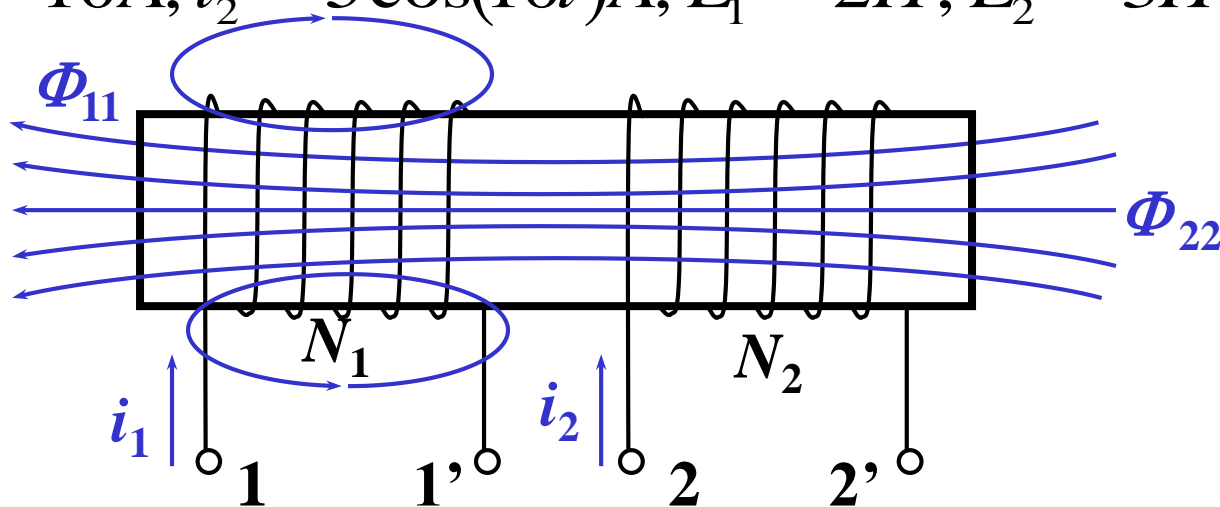例10-1: 互感耦合电路中,求两耦合线圈中的磁通链。

$$i_1 = 10A, i_2 = 5\cos(10t)A, L_1 = 2H, L_2 = 3H, M = 1H$$




解


$$\Psi_1 = \Psi_{11} + \Psi_{12} = L_1 i_1 + M i_2 = 20 + 5\cos(10t) \text{ Wb}$$

$$\Psi_2 = \Psi_{21} + \Psi_{22} = L_2 i_2 + M i_1 = 10 + 15\cos(10t) \text{ Wb}$$

例10-2: 线圈的绕向及相互位置如下图，判断同名端

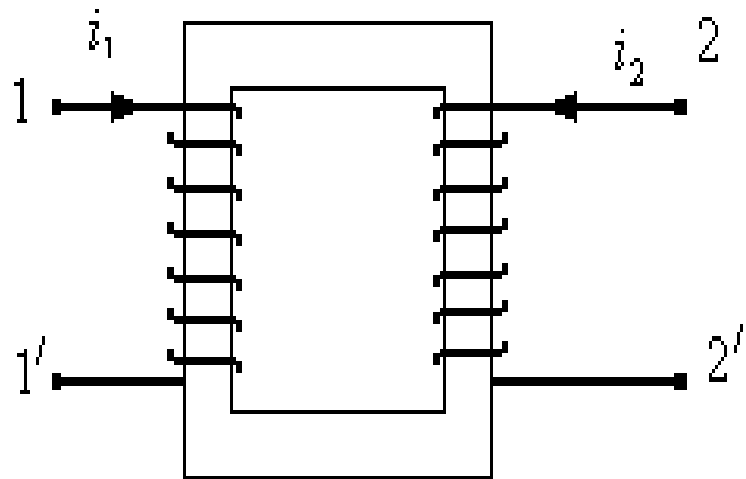


M 前面为正

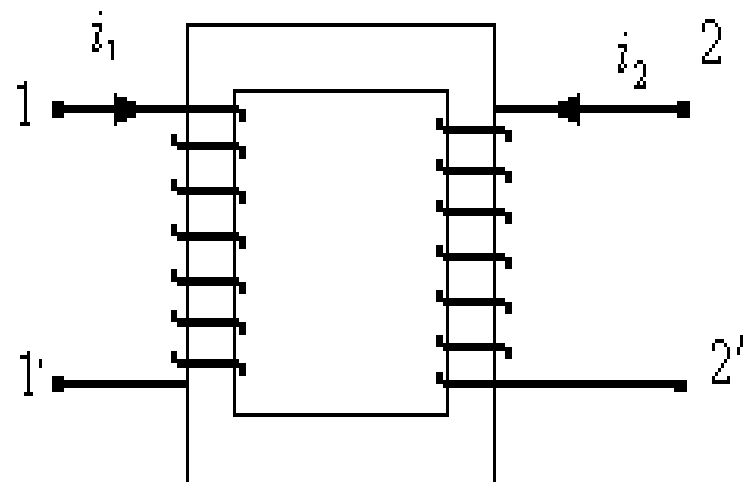

M 前面为负

三、耦合线圈中的感应电压

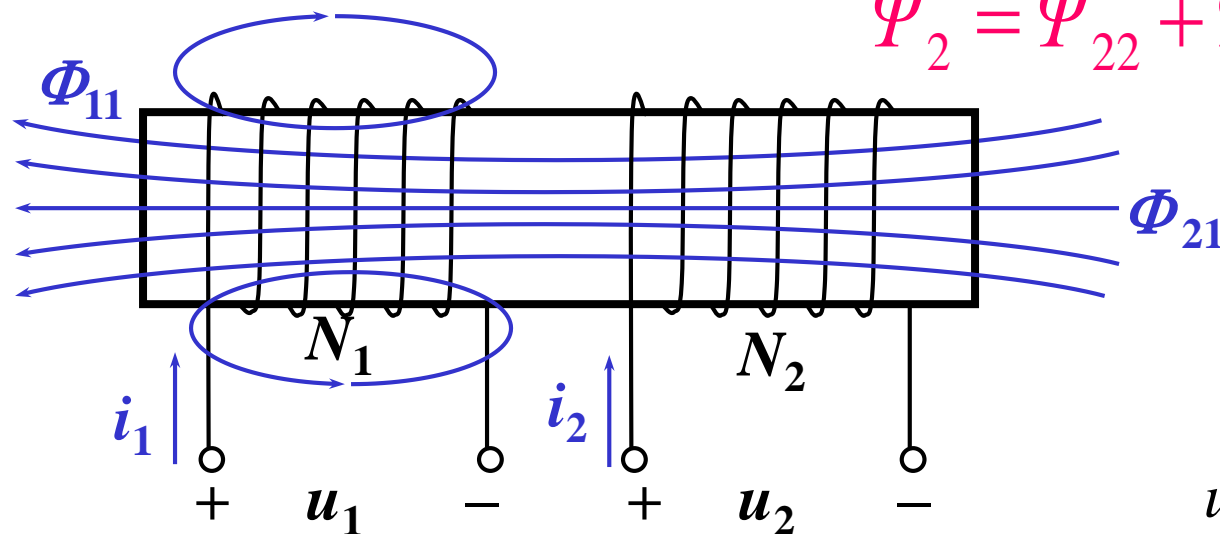

$$\Psi_1 = \Psi_{11} + \Psi_{12} = L_1 i_1 \pm M_{12} i_2$$

$$\Psi_2 = \Psi_{22} + \Psi_{21} = L_2 i_2 \pm M_{21} i_1$$

自感电压

$$u_{11} = \frac{d\Psi_{11}}{dt} = L_1 \frac{di_1}{dt}$$

互感电压

$$u_{12} = \frac{d\Psi_{12}}{dt} = M_{12} \frac{di_2}{dt}$$

$$u_1 = \frac{d\Psi_1}{dt} = L_1 \frac{di_1}{dt} \pm M \frac{di_2}{dt}$$

$$u_2 = \frac{d\Psi_2}{dt} = L_2 \frac{di_2}{dt} \pm M \frac{di_1}{dt}$$


相量形式:

$$\dot{U}_1 = j\omega L_1 \dot{I}_1 \pm j\omega M_{12} \dot{I}_2$$

$$\dot{U}_2 = j\omega L_2 \dot{I}_2 \pm j\omega M_{21} \dot{I}_1$$

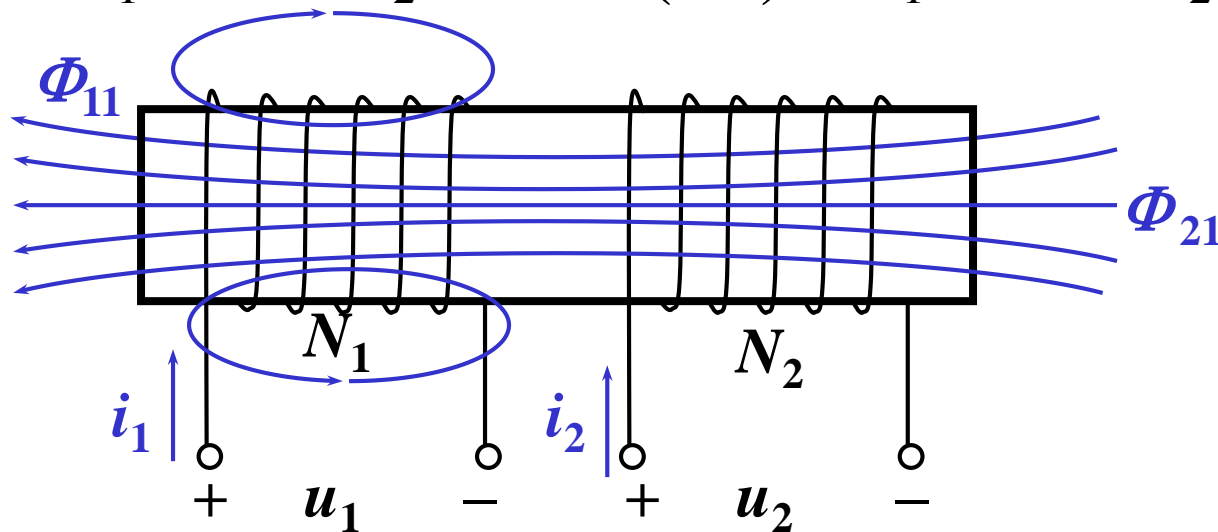例10-3: 互感耦合电路中,求两耦合线圈的端电压。

$$i_1 = 10A, i_2 = 5\cos(10t)A, L_1 = 2H, L_2 = 3H, M = 1H$$



解

$$u_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} = -50 \sin(10t) V$$

互感电压

$$u_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} = -150 \sin(10t) V$$

自感电压

“点”符号与同名端

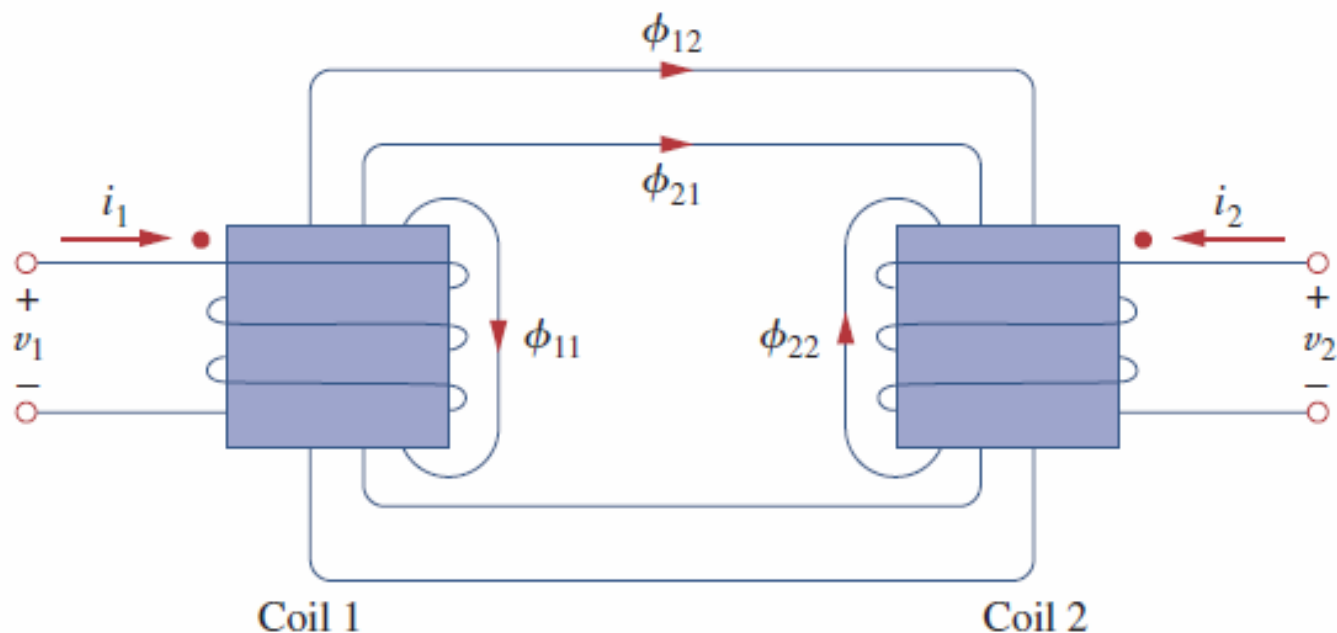


Figure 13.4


Illustration of the dot convention.

If a current **enters** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **positive** at the dotted terminal of the second coil.


Dot convention

Alternatively,

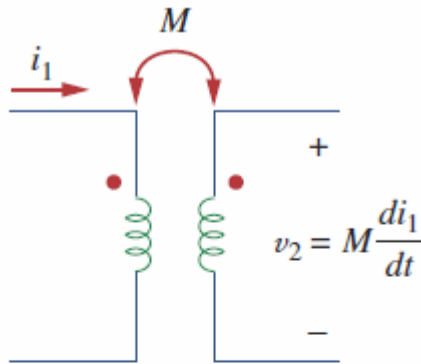
If a current **leaves** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **negative** at the dotted terminal of the second coil.




(a)

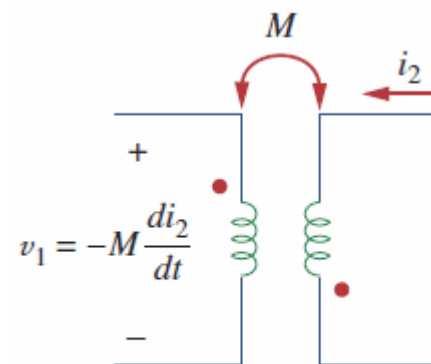

(c)

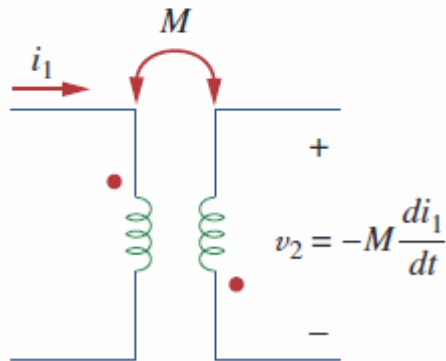


(b)

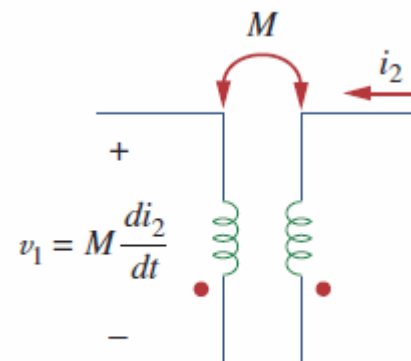


(d)

例10-4: 根据图中“同名端”，写出感应电压表达式。

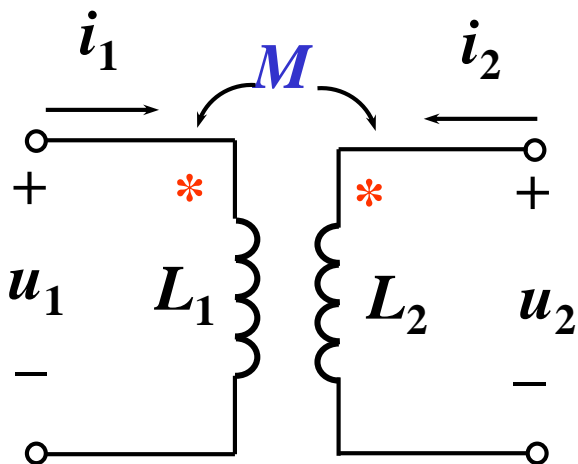


$$u_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$
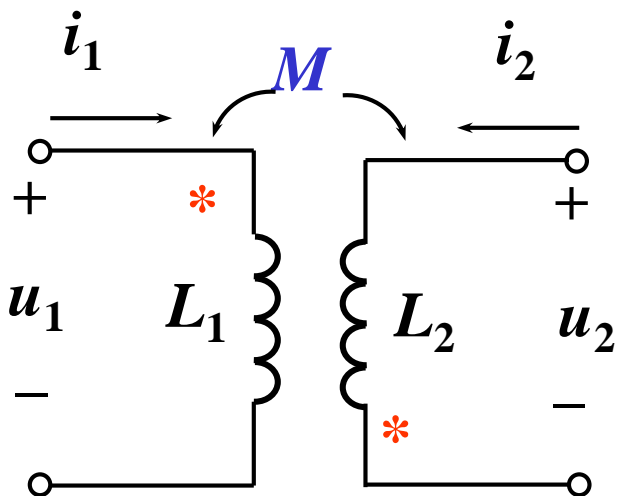
$$u_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$




$$u_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$
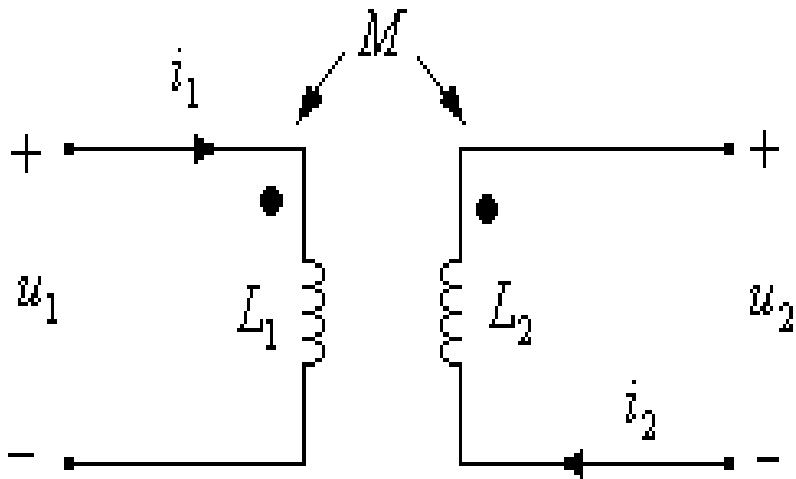
$$u_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$




$$u_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$
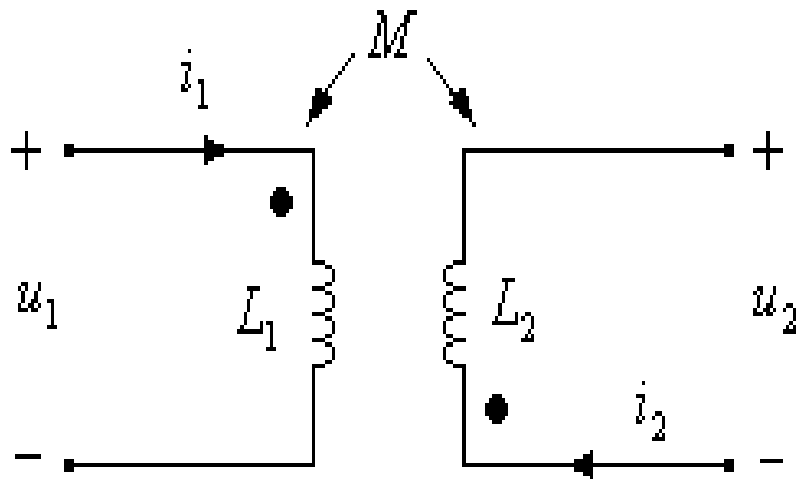
$$u_2 = -L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$




$$u_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

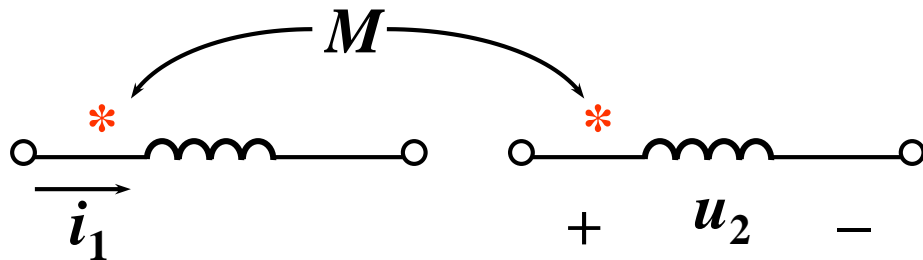
$$u_2 = -L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$



$$u_2 = M \frac{di_1}{dt}$$

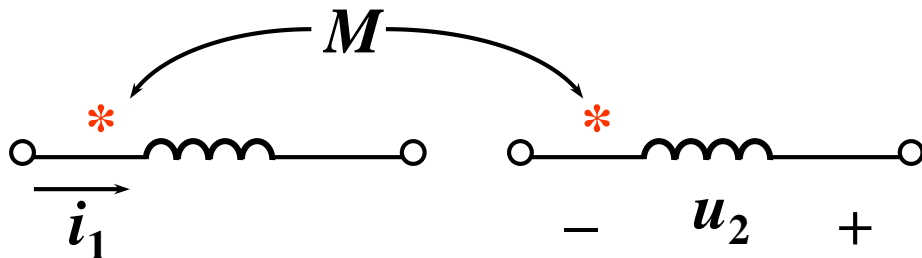

$$u_2 = -M \frac{di_1}{dt}$$

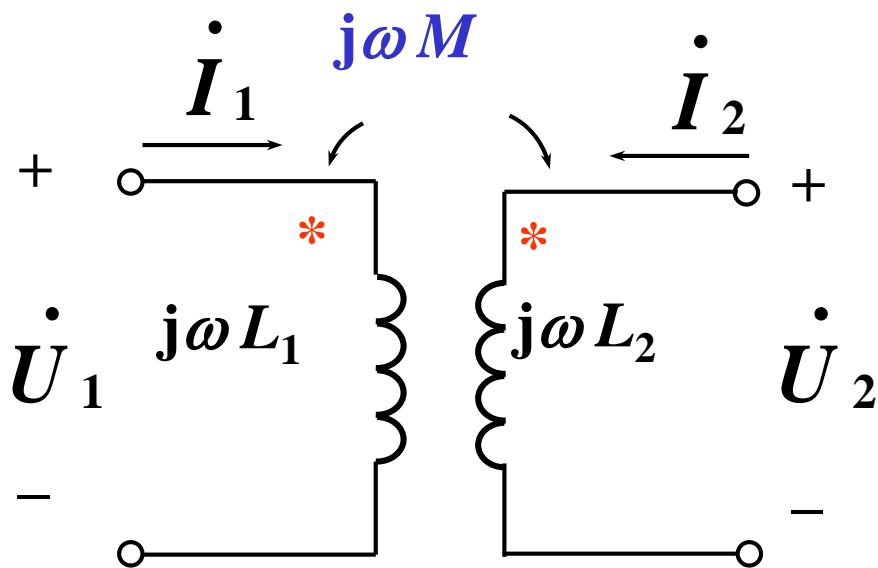


$$\dot{U}_1 = j\omega L_1 \dot{I}_1 + j\omega M \dot{I}_2$$

$$\dot{U}_2 = j\omega M \dot{I}_1 + j\omega L_2 \dot{I}_2$$


ωM : 互感抗

四、耦合电感的等效受控源电路

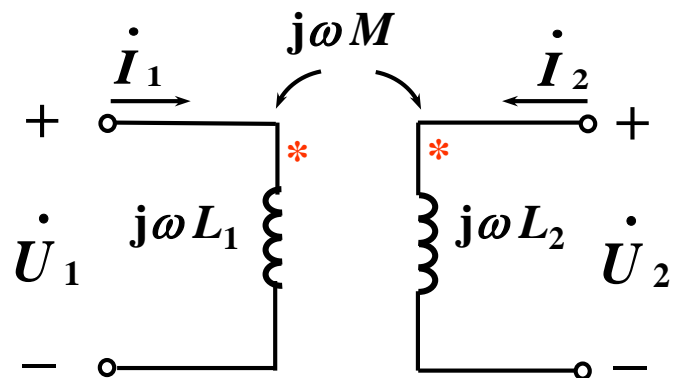


$$\dot{U}_1 = \dot{U}_{11} + \dot{U}_{12}$$
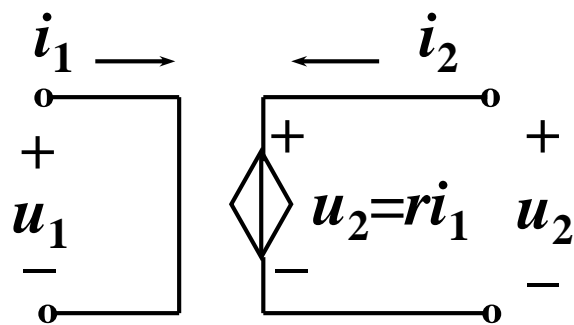
$$\dot{U}_2 = \dot{U}_{22} + \dot{U}_{21}$$



CCVS

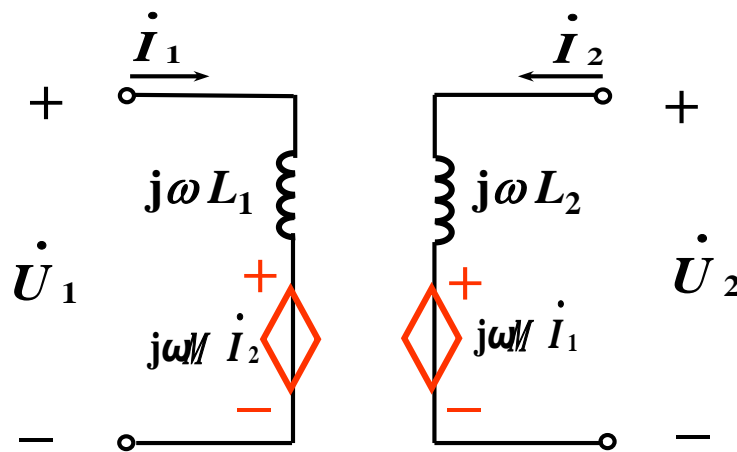


五、耦合因数


$$K \stackrel{\text{def}}{=} \sqrt{\frac{|\Psi_{12}\Psi_{21}|}{\Psi_{11}\Psi_{22}}} \Rightarrow K \stackrel{\text{def}}{=} \frac{M}{\sqrt{L_1 L_2}} \leq 1$$

k=1
全耦合

顺序相连（串联）的耦合电感

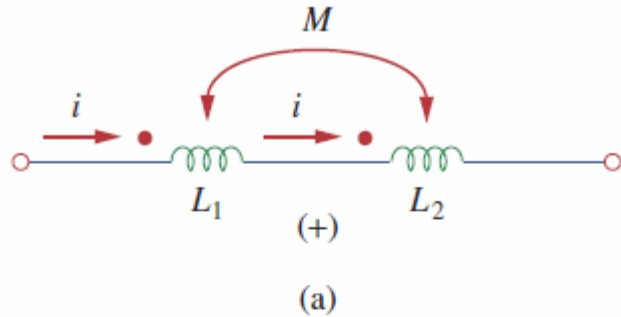
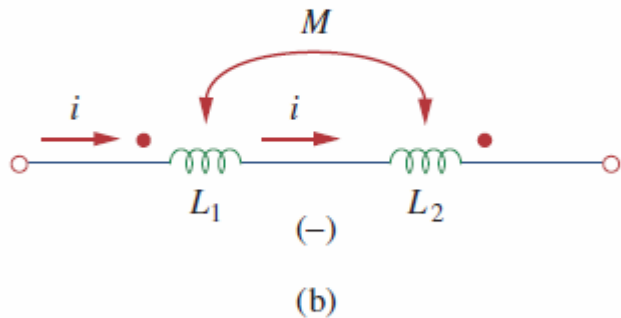
$$L = L_1 + L_2 + 2M \quad (\text{Series-aiding connection})$$



$$L = L_1 + L_2 - 2M \quad (\text{Series-opposing connection})$$


Figure 13.6

Dot convention for coils in series; the sign indicates the polarity of the mutual voltage: (a) series-aiding connection, (b) series-opposing connection.

§ 10-2 含有耦合电感电路的计算

一、互感线圈的串联


a、顺向串联

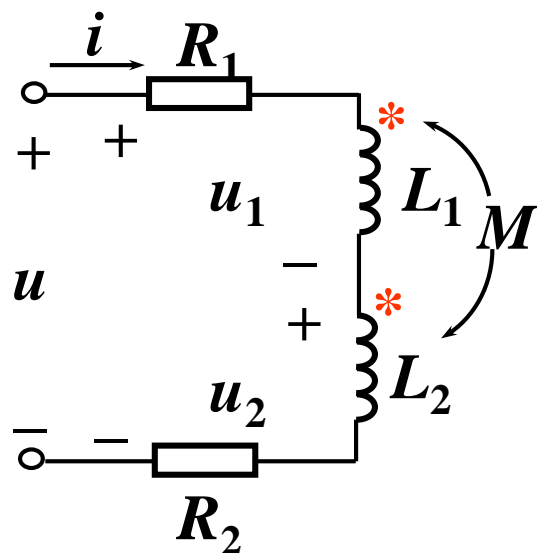

$$u = u_1 + u_2$$


$$= R_1 i + L_1 \frac{di}{dt} + M \frac{di}{dt} + L_2 \frac{di}{dt} + M \frac{di}{dt} + R_2 i$$
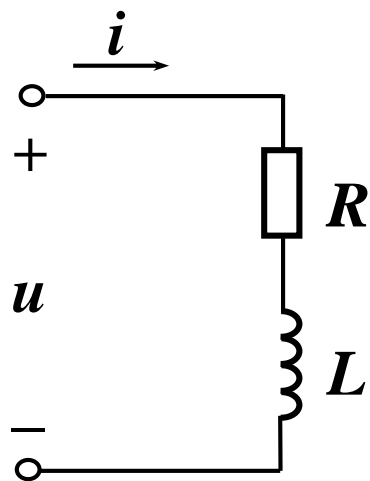
$$= (R_1 + R_2) i + (L_1 + L_2 + 2M) \frac{di}{dt}$$




$$R_{eq} = R_1 + R_2$$

$$L_{eq} = L_1 + L_2 + 2M$$

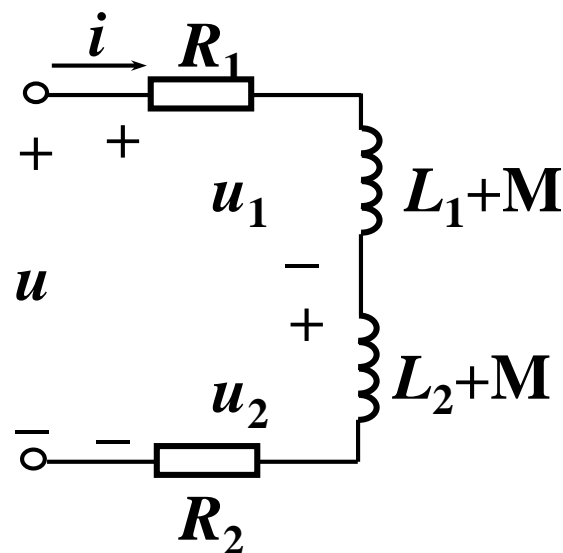

b、反向串联

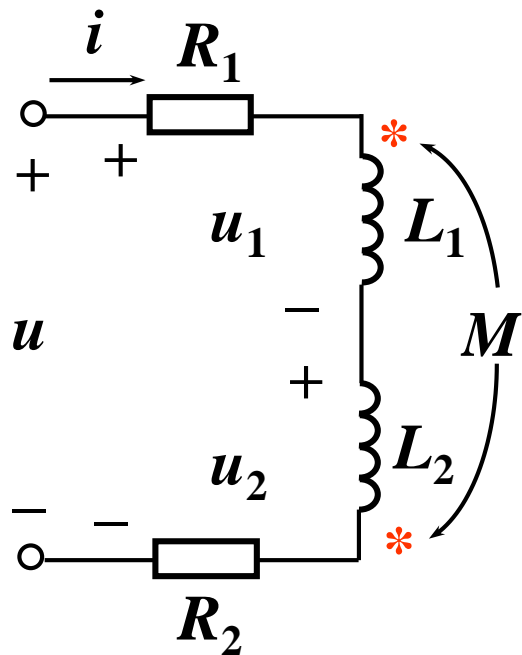

$$u = u_1 + u_2$$



$$= R_1 i + L_1 \frac{di}{dt} - M \frac{di}{dt} + L_2 \frac{di}{dt} - M \frac{di}{dt} + R_2 i$$

$$= (R_1 + R_2) i + (L_1 + L_2 - 2M) \frac{di}{dt}$$

$$R_{eq} = R_1 + R_2$$

$$L_{eq} = L_1 + L_2 - 2M$$
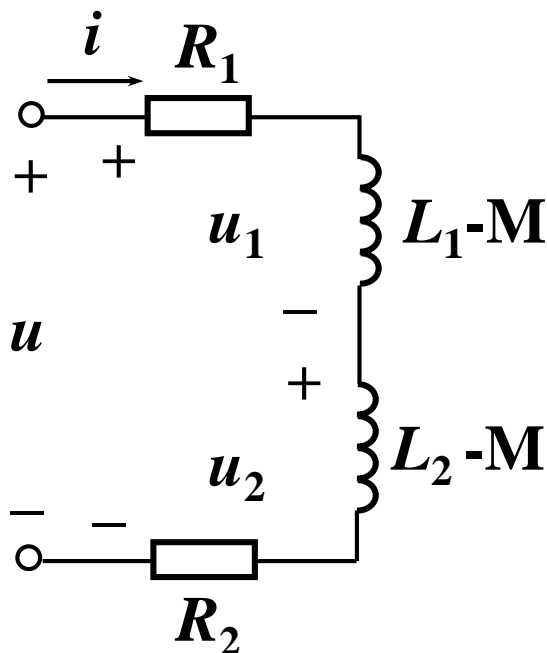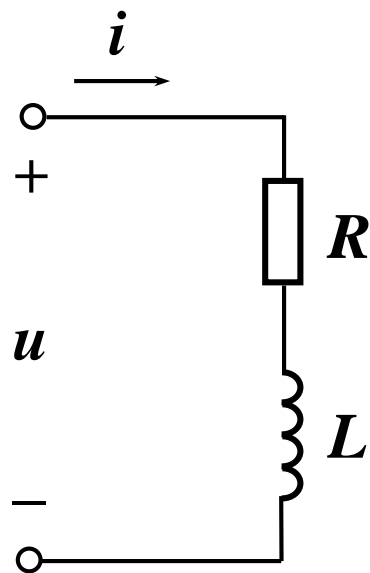
$$\therefore M \leq \frac{1}{2}(L_1 + L_2)$$




互感的测量方法：



• 顺接一次，反接一次，
就可以测出互感：

$$M = \frac{L_{\text{顺}} - L_{\text{反}}}{4}$$


在正弦激励下：

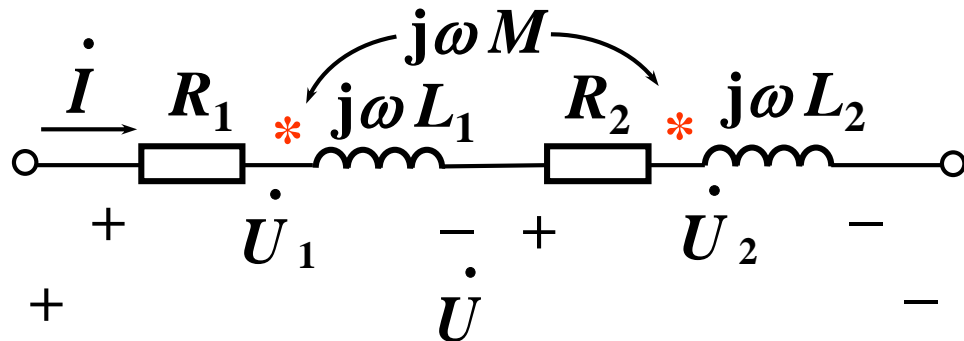
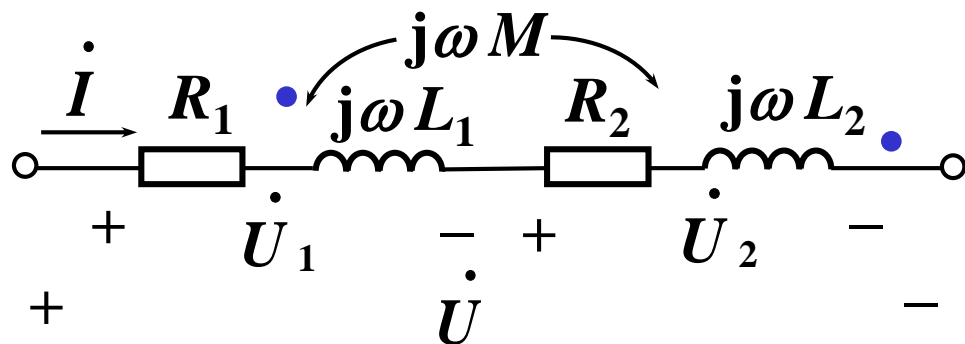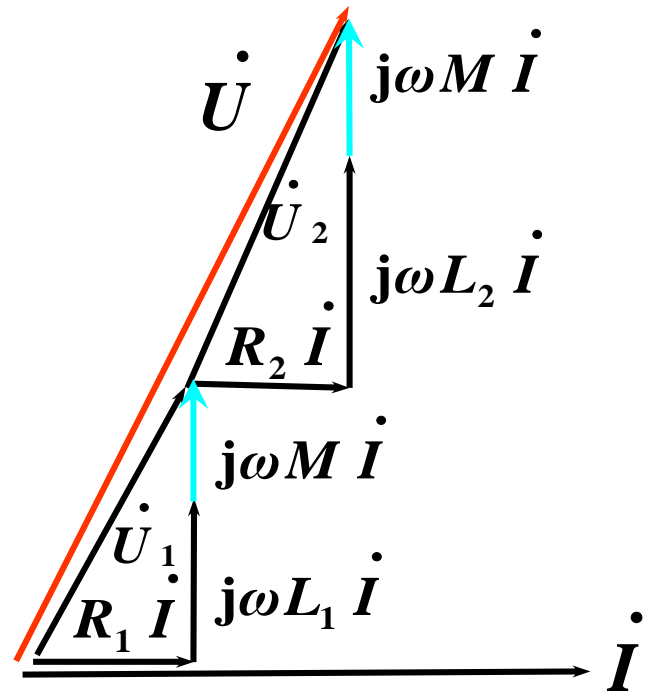
$$\dot{U} = (R_1 + R_2) \dot{I} + j\omega(L_1 + L_2 + 2M) \dot{I}$$



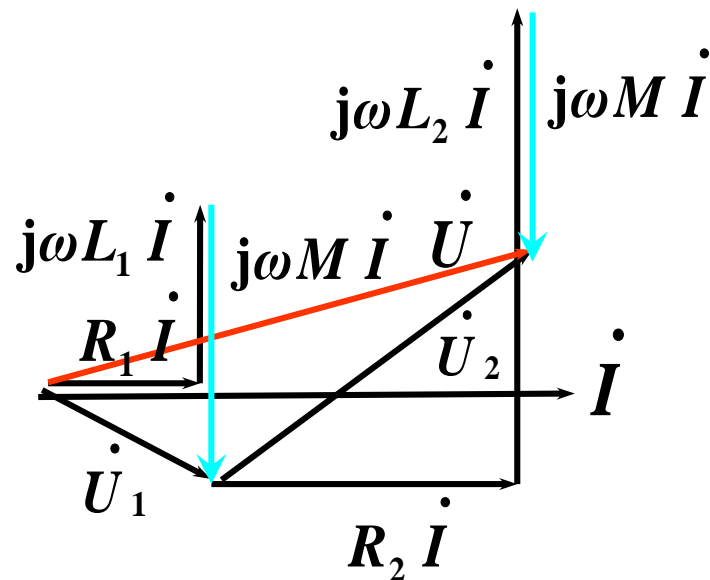
$$\dot{U} = (R_1 + R_2) \dot{I} + j\omega(L_1 + L_2 - 2M) \dot{I}$$



二、互感线圈的并联

a、同侧并联

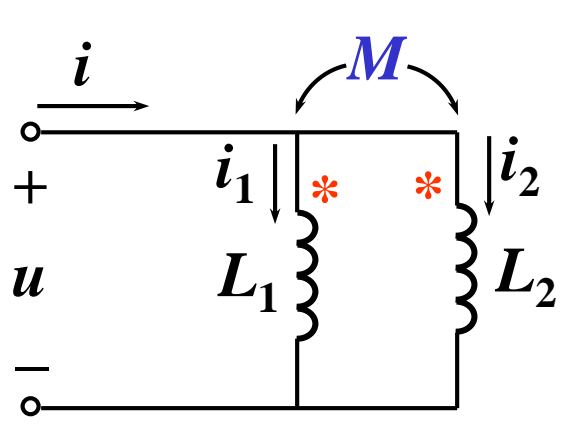

$$u = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$u = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$i = i_1 + i_2$$


$$u = (L_1 - M) \frac{di_1}{dt} + M \frac{di}{dt}$$

$$u = (L_2 - M) \frac{di_2}{dt} + M \frac{di}{dt}$$


$$u = \frac{(L_1 L_2 - M^2)}{L_1 + L_2 - 2M} \frac{di}{dt}$$

$$L_{eq} = \frac{(L_1 L_2 - M^2)}{L_1 + L_2 - 2M} \geq 0$$

$$M \leq \sqrt{L_1 L_2}$$

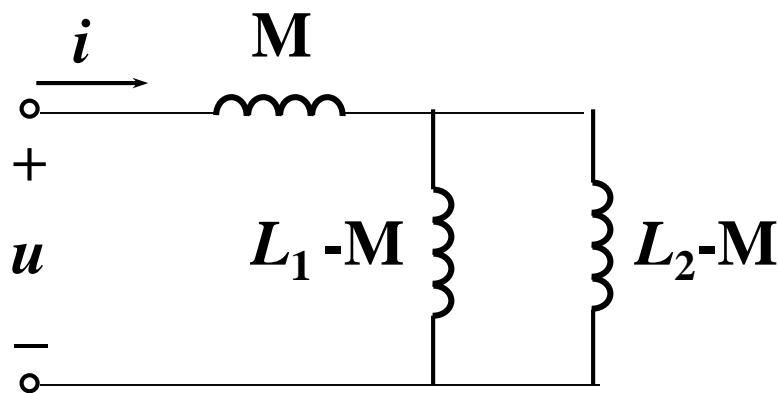

b、异侧并联

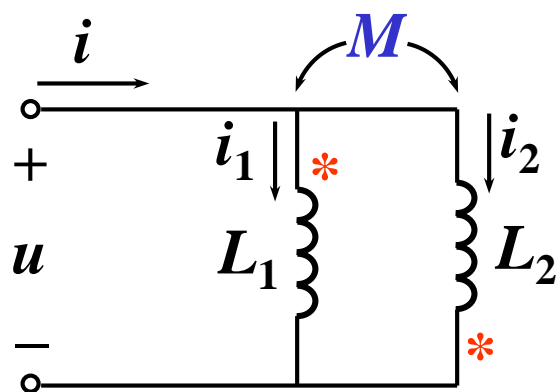


$$\begin{cases} u = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} \\ u = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} \\ i = i_1 + i_2 \end{cases}$$

$$u = (L_1 + M) \frac{di_1}{dt} - M \frac{di}{dt}$$

$$u = (L_2 + M) \frac{di_2}{dt} - M \frac{di}{dt}$$



$$u = \frac{(L_1 L_2 - M^2)}{L_1 + L_2 + 2M} \frac{di}{dt}$$
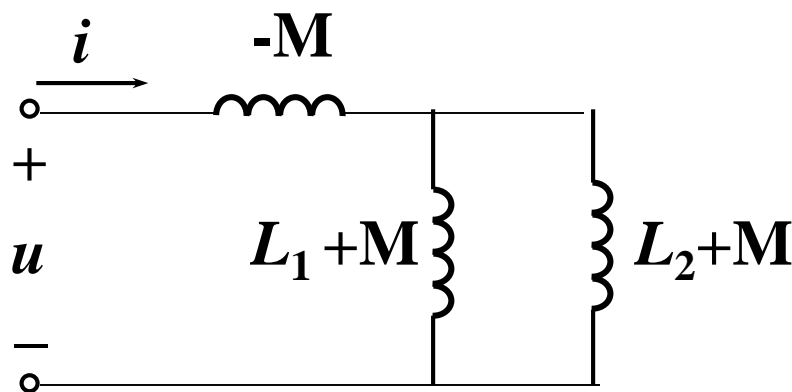
$$L_{eq} = \frac{(L_1 L_2 - M^2)}{L_1 + L_2 + 2M} \geq 0$$



三、有公共端的耦合电感的T型等效电路

(a) 同名端接在一起



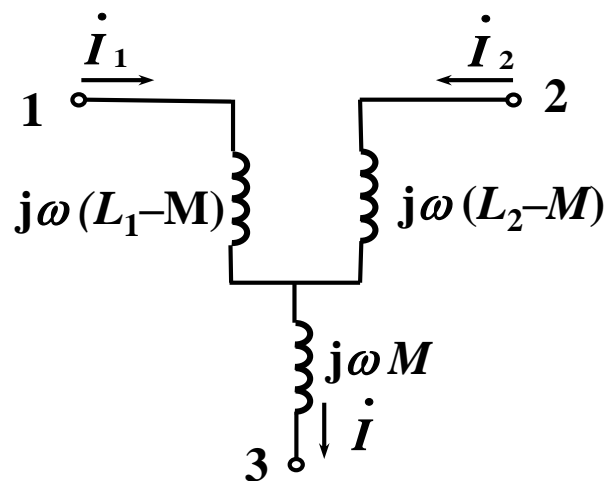
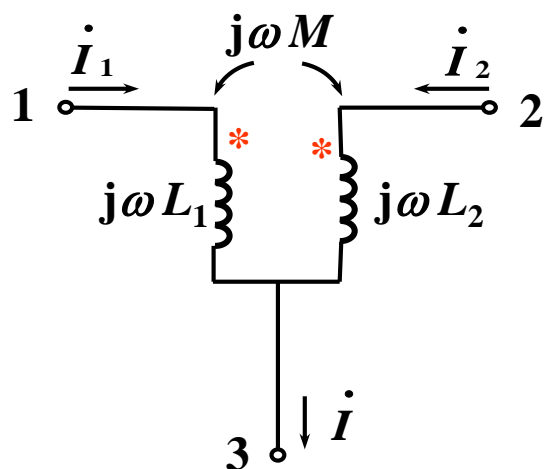


$$\begin{cases} \dot{U}_{13} = j\omega L_1 \dot{I}_1 + j\omega M \dot{I}_2 \\ \dot{U}_{23} = j\omega L_2 \dot{I}_2 + j\omega M \dot{I}_1 \\ \dot{I} = \dot{I}_1 + \dot{I}_2 \end{cases}$$



整理得


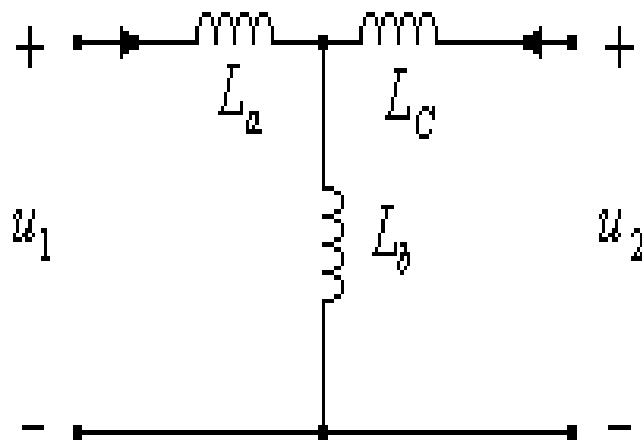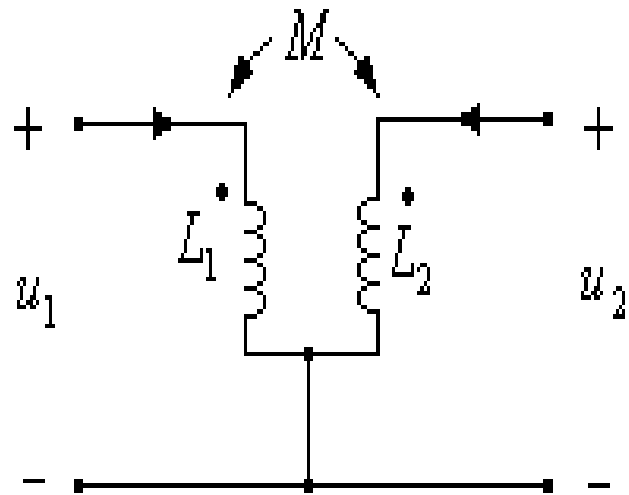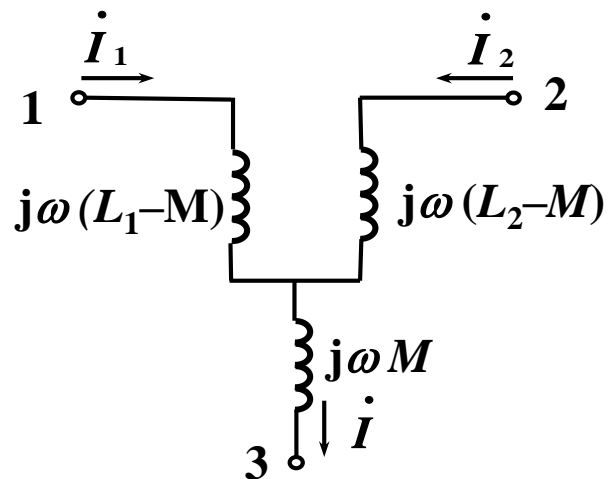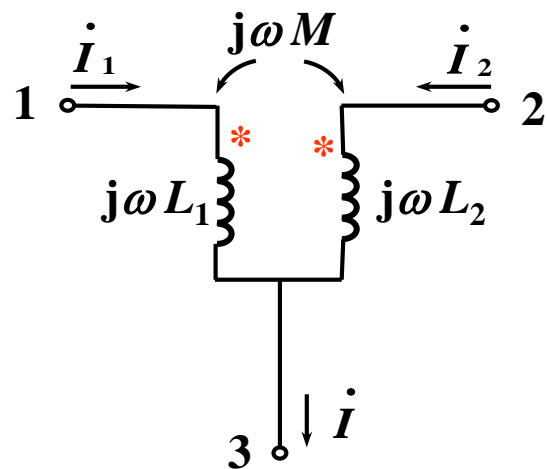
$$\begin{cases} \dot{U}_{13} = j\omega(L_1 - M) \dot{I}_1 + j\omega M \dot{I} \\ \dot{U}_{23} = j\omega(L_2 - M) \dot{I}_2 + j\omega M \dot{I} \end{cases}$$



(b) 非同名端接在一起



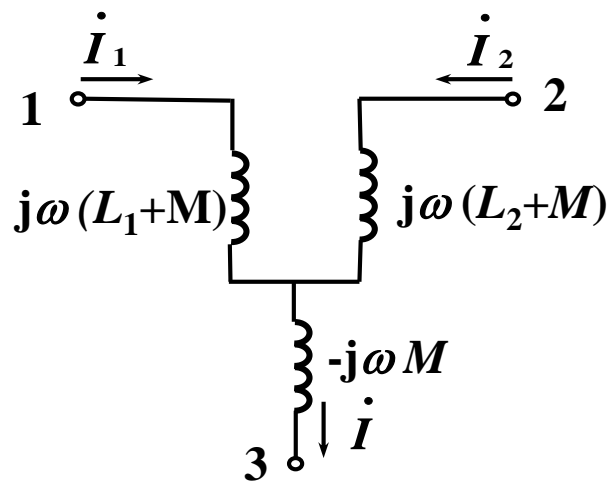
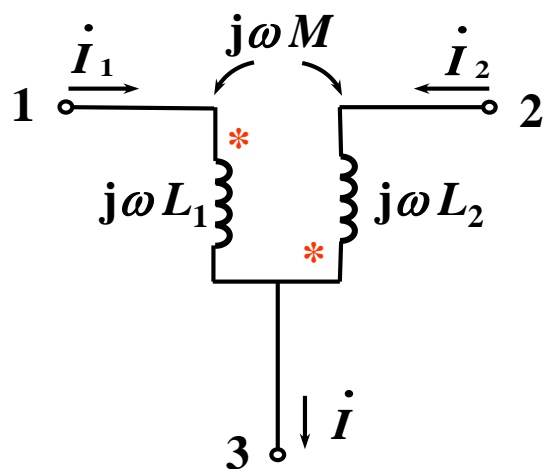


$$\begin{cases} \dot{U}_{13} = j\omega L_1 \dot{I}_1 - j\omega M \dot{I}_2 \\ \dot{U}_{23} = j\omega L_2 \dot{I}_2 - j\omega M \dot{I}_1 \\ \dot{I} = \dot{I}_1 + \dot{I}_2 \end{cases}$$

整理得


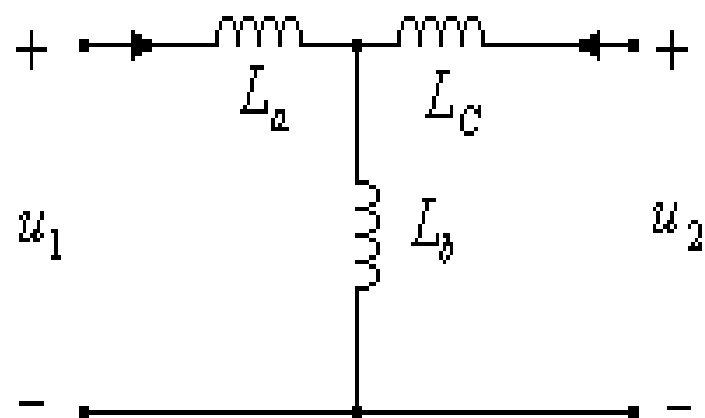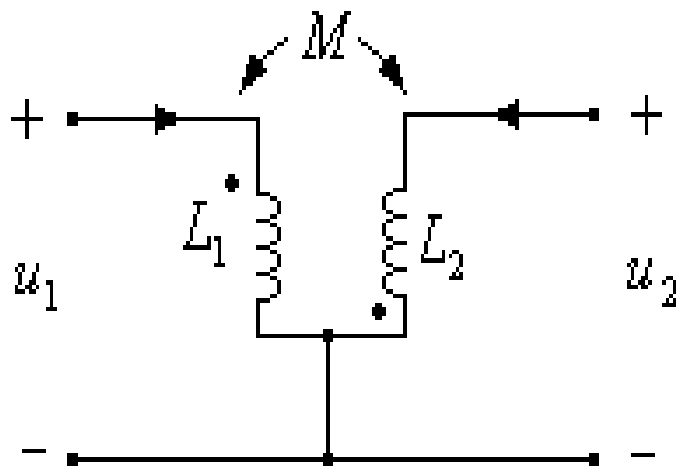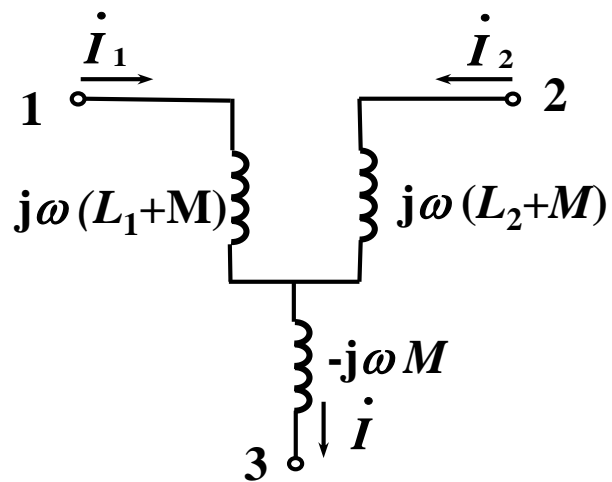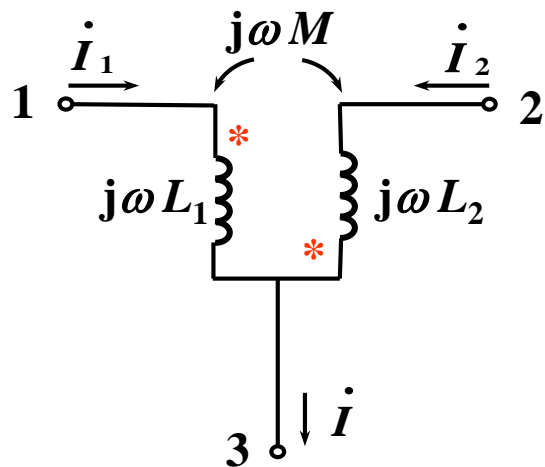
$$\begin{cases} \dot{U}_{13} = j\omega(L_1 + M) \dot{I}_1 - j\omega M \dot{I} \\ \dot{U}_{23} = j\omega(L_2 + M) \dot{I}_2 - j\omega M \dot{I} \end{cases}$$



变压器


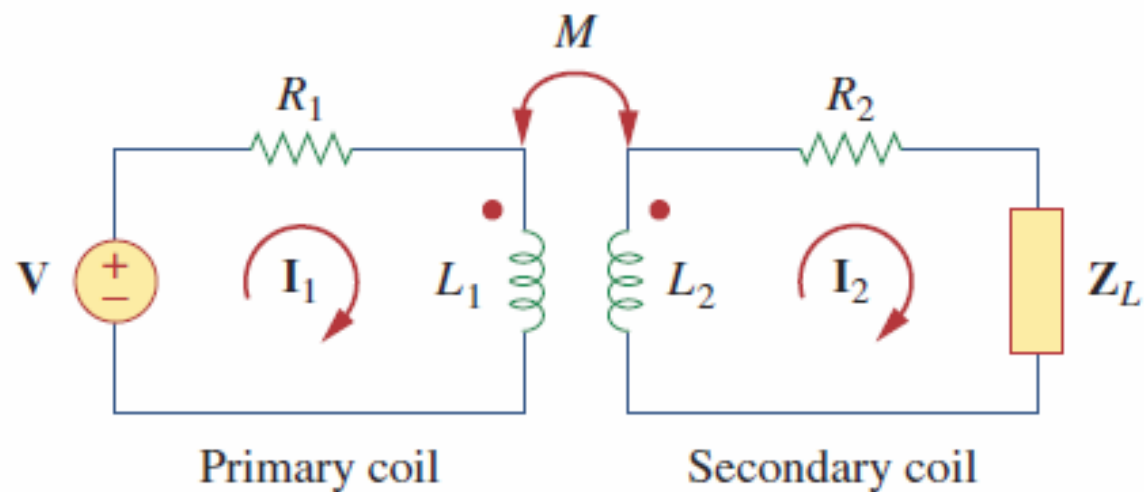


Figure 13.19
A linear transformer.

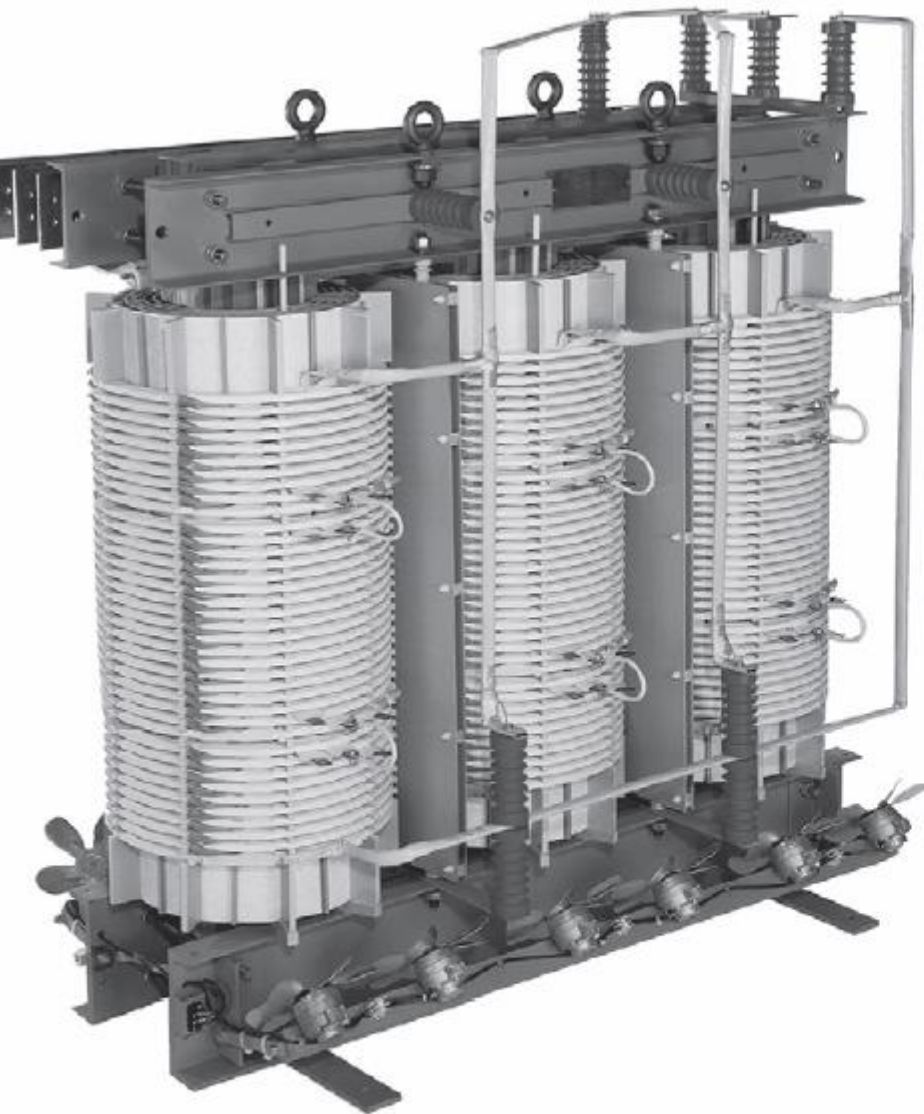

(a)




(b)

Figure 13.20

different types of transformers: (a) copper wound dry power transformer, (b) audio transformers.

Courtesy of: (a) Electric Service Co., (b) Jensen Transformers.

理想变压器

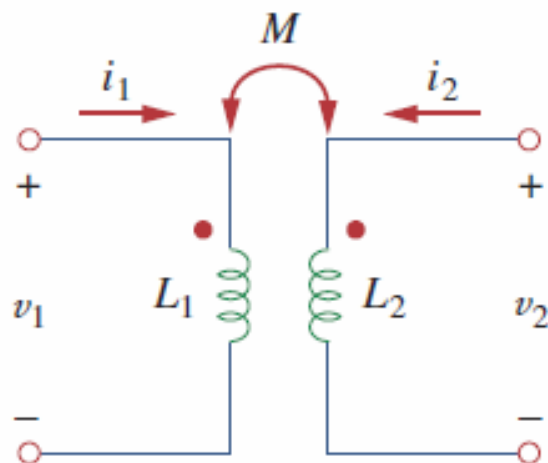

$$\mathbf{V}_1 = j\omega L_1 \mathbf{I}_1 + j\omega M \mathbf{I}_2$$

$$\mathbf{V}_2 = j\omega M \mathbf{I}_1 + j\omega L_2 \mathbf{I}_2$$

$$\mathbf{I}_1 = (\mathbf{V}_1 - j\omega M \mathbf{I}_2) / j\omega L_1$$

$$\mathbf{V}_2 = j\omega L_2 \mathbf{I}_2 + \frac{M \mathbf{V}_1}{L_1} - \frac{j\omega M^2 \mathbf{I}_2}{L_1}$$

$M = \sqrt{L_1 L_2}$ for perfect coupling ($k = 1$). Hence,

$$\mathbf{V}_2 = j\omega L_2 \mathbf{I}_2 + \frac{\sqrt{L_1 L_2} \mathbf{V}_1}{L_1} - \frac{j\omega L_1 L_2 \mathbf{I}_2}{L_1} = \sqrt{\frac{L_2}{L_1}} \mathbf{V}_1 = n \mathbf{V}_1$$

A transformer is said to be ideal if it has the following properties:

1. Coils have very large reactances ($L_1, L_2, M \rightarrow \infty$).
2. Coupling coefficient is equal to unity ($k = 1$).
3. Primary and secondary coils are lossless ($R_1 = 0 = R_2$).

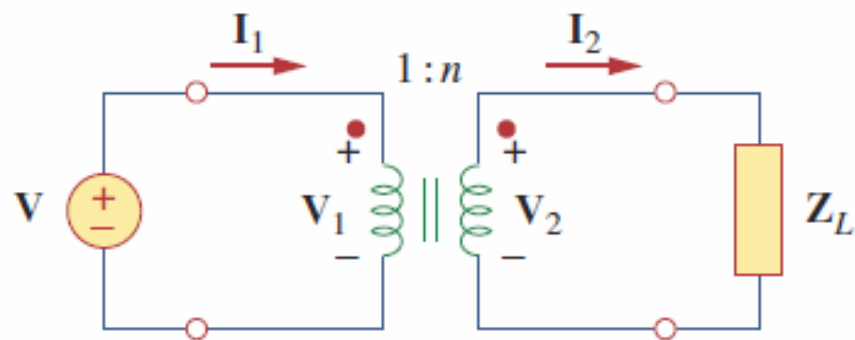


Figure 13.31

Relating primary and secondary quantities in an ideal transformer.

$$v_1 = N_1 \frac{d\phi}{dt}$$

$$v_2 = N_2 \frac{d\phi}{dt}$$

$$\frac{v_2}{v_1} = \frac{N_2}{N_1} = n$$

$$\frac{\mathbf{V}_2}{\mathbf{V}_1} = \frac{N_2}{N_1} = n$$


$$v_1 i_1 = v_2 i_2$$

$$\frac{\mathbf{I}_1}{\mathbf{I}_2} = \frac{\mathbf{V}_2}{\mathbf{V}_1} = n$$


$$\frac{\mathbf{I}_2}{\mathbf{I}_1} = \frac{N_1}{N_2} = \frac{1}{n}$$

如何确定n 的正负号

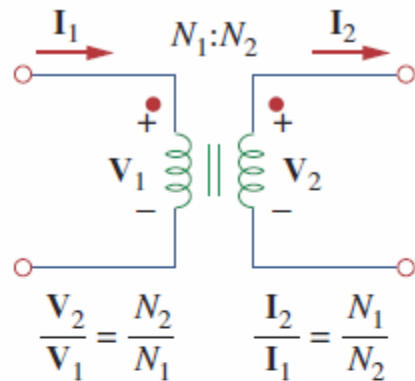
1. If \mathbf{V}_1 and \mathbf{V}_2 are *both* positive or both negative at the dotted terminals, use $+n$ in Eq. (13.52). Otherwise, use $-n$.
2. If \mathbf{I}_1 and \mathbf{I}_2 *both* enter into or both leave the dotted terminals, use $-n$ in Eq. (13.55). Otherwise, use $+n$.




(a)

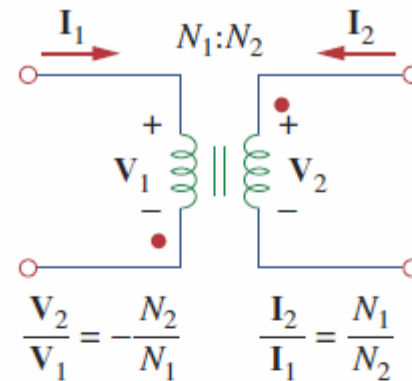

(c)

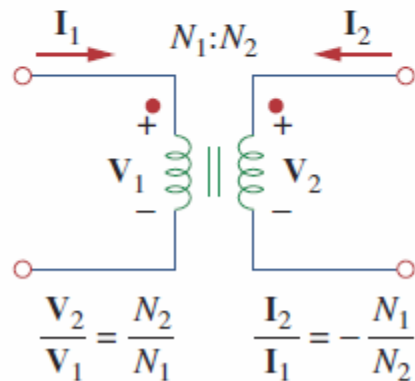

(b)

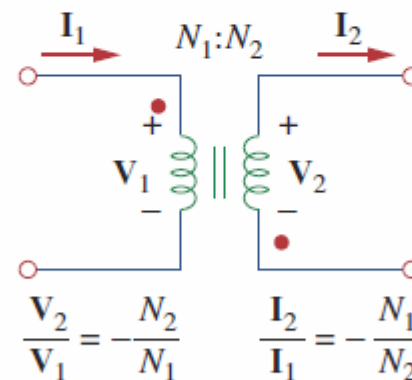


(d)


Figure 13.32

Typical circuits illustrating proper voltage polarities and current directions in an ideal transformer.

§ 10-3 理想变压器

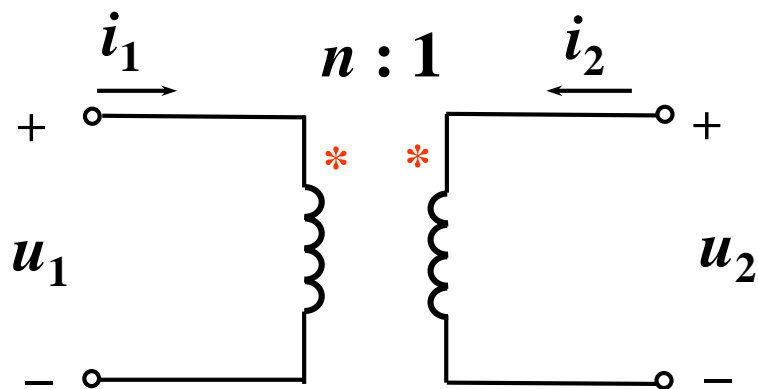

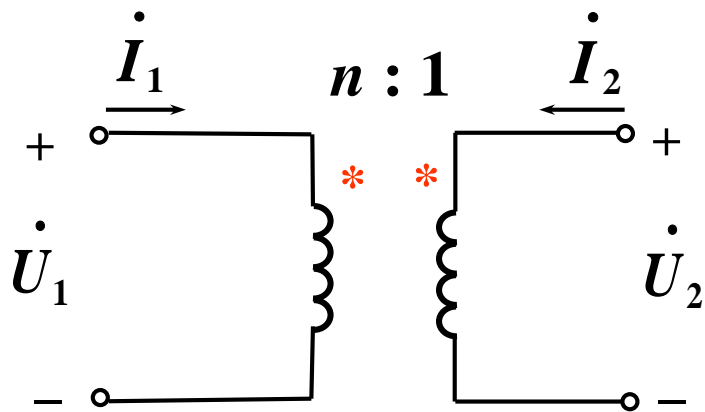
$$\begin{cases} u_1 = n u_2 \\ i_1 = -\frac{1}{n} i_2 \end{cases}$$



$$\begin{cases} \dot{U}_1 = n \dot{U}_2 \\ \dot{I}_1 = -\frac{1}{n} \dot{I}_2 \end{cases}$$

理想变压器的性质：


(a) 阻抗变换性质

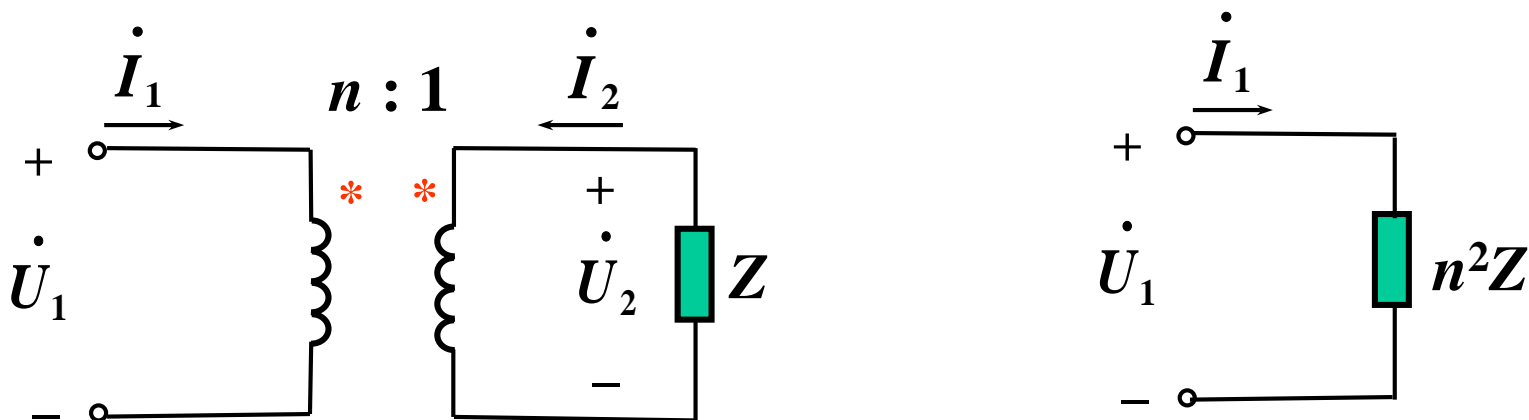

$$\frac{\dot{U}_1}{\dot{I}_1} = \frac{n\dot{U}_2}{-1/n\dot{I}_2} = n^2 \left(-\frac{\dot{U}_2}{\dot{I}_2} \right) = n^2 Z$$

(b) 功率性质：


理想变压器的特性方程为代数关系，因此无记忆作用。

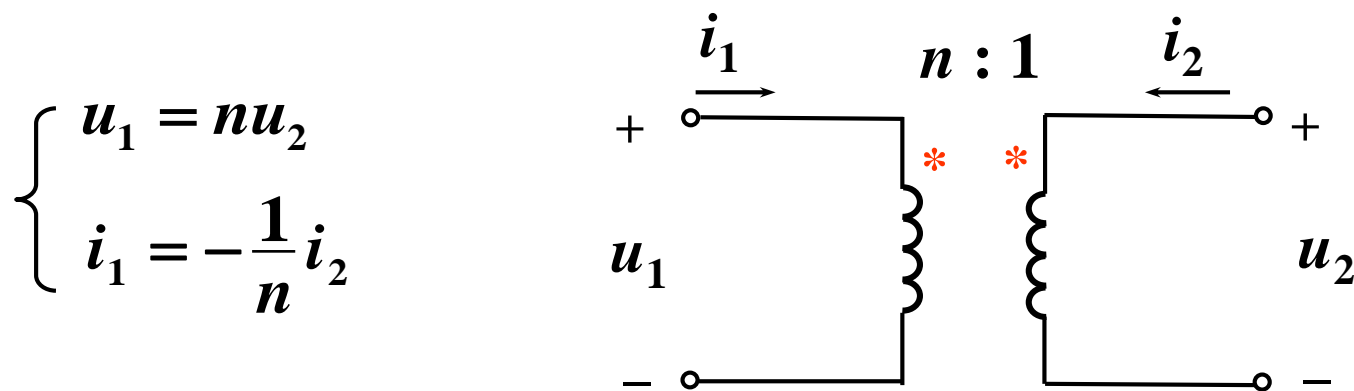

$$p = u_1 i_1 + u_2 i_2 = u_1 i_1 + \frac{1}{n} u_1 \times (-n i_1) = 0$$

由此可以看出，理想变压器既不储能，也不耗能，在电路中只起传递信号和能量的作用。

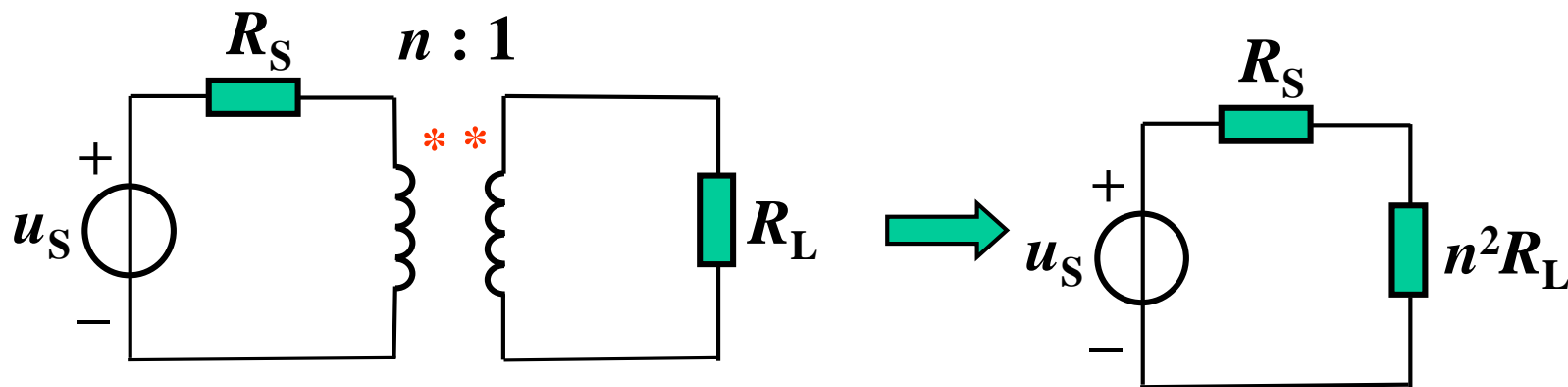例10-9. 已知电源内阻 $R_S=1\text{k}\Omega$ ，负载电阻 $R_L=10\Omega$ 。为使 R_L 上获得最大功率，求理想变压器的变比 n 。



解：

当 $n^2 R_L = R_S$ 时匹配，即

$$10n^2 = 1000$$

$$\therefore n^2 = 100, \quad n = 10.$$

阻抗匹配(impedance matching)

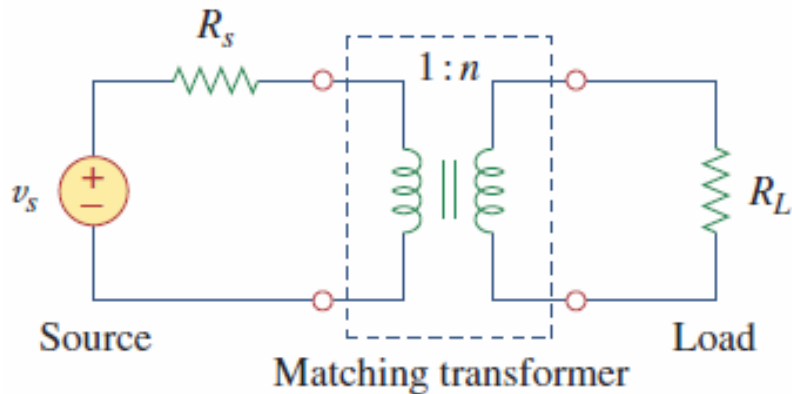


Figure 13.64

Transformer used as a matching device.

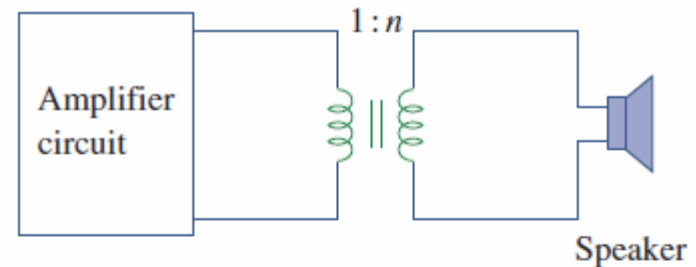


Figure 13.65

Using an ideal transformer to match the speaker to the amplifier; for Example 13.16.


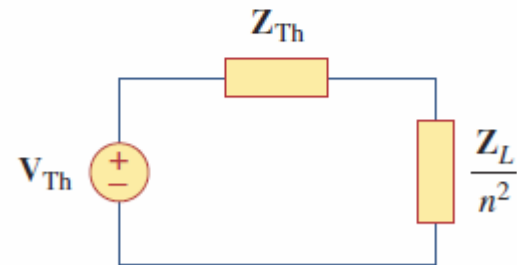


Figure 13.66

Equivalent circuit of the circuit in Fig. 13.65; for Example 13.16.

例10-4. 求 \dot{U}_2 .

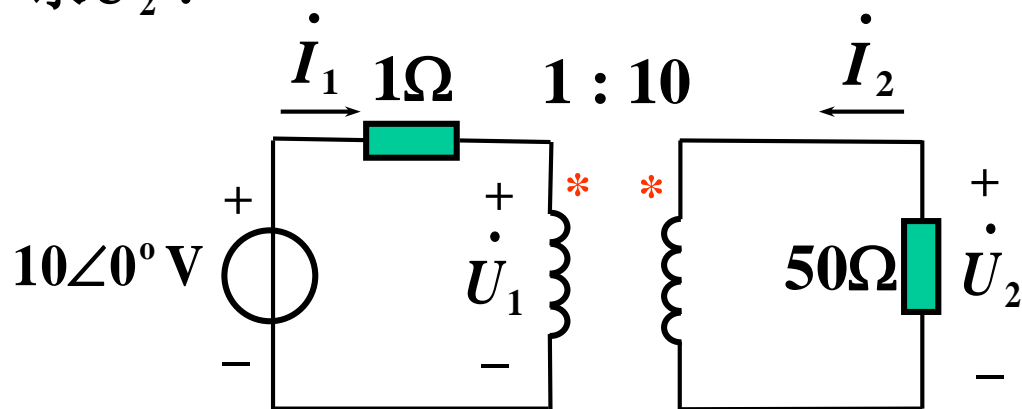

方法1: 列方程


$$\begin{cases} 1 \times \dot{I}_1 + \dot{U}_1 = 10\angle 0^\circ \\ 50\dot{I}_2 + \dot{U}_2 = 0 \\ \dot{U}_1 = \frac{1}{10}\dot{U}_2 \\ \dot{I}_1 = -10\dot{I}_2 \end{cases}$$

解得



$$\dot{U}_2 = 33.33\angle 0^\circ \text{ V}$$


方法2：阻抗变换

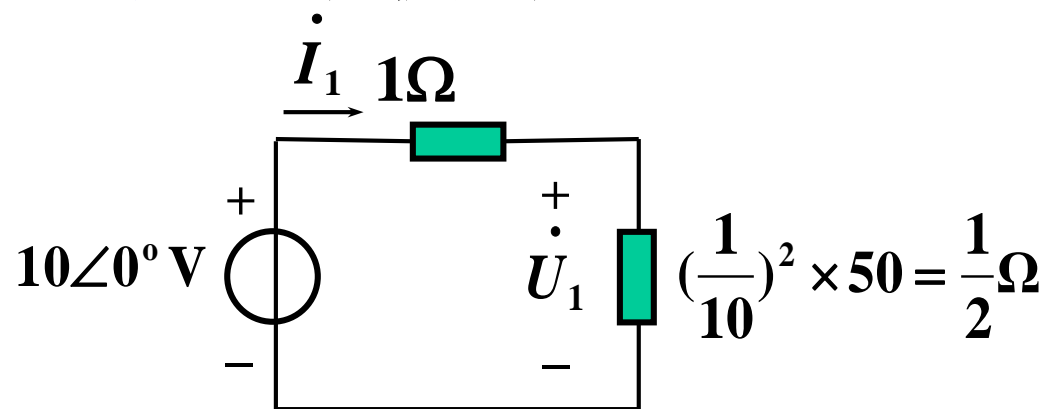

$$\dot{U}_1 = \frac{10\angle 0^\circ}{1 + 1/2} \times \frac{1}{2} = \frac{10}{3} \angle 0^\circ \text{ V}$$

$$\begin{aligned} \dot{U}_2 &= n\dot{U}_1 = 10\dot{U}_1 \\ &= 33.33\angle 0^\circ \text{ V} \end{aligned}$$

例10-5.

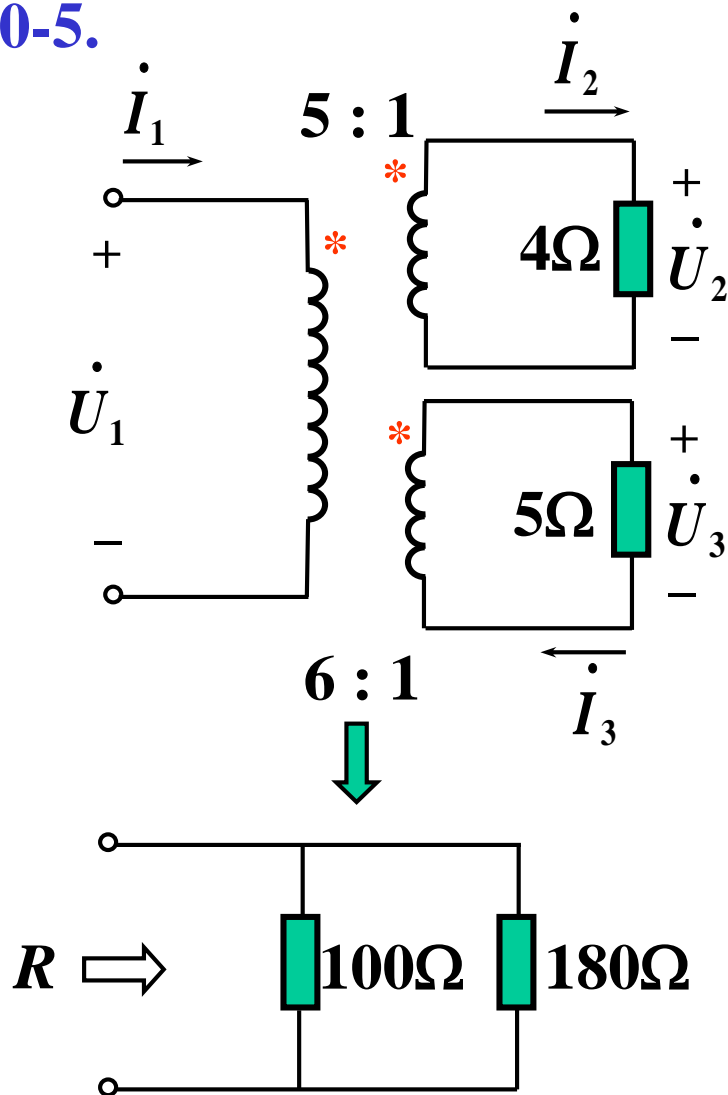

$$\therefore R = 100 // 180 = 64.3\Omega$$

理想变压器副边有两个线圈，
变比分别为5:1和6:1。

求原边等效电阻 R 。

两个副边并联原边

解：

$$\dot{I}_1 = \frac{1}{5}\dot{I}_2 + \frac{1}{6}\dot{I}_3$$

$$\dot{U}_1 = 5\dot{U}_2, \quad \dot{U}_1 = 6\dot{U}_3$$

$$\begin{aligned} R &= \frac{\dot{U}_1}{\dot{I}_1} = \frac{\dot{U}_1}{\frac{1}{5}\dot{I}_2 + \frac{1}{6}\dot{I}_3} = \frac{\dot{U}_1}{\frac{1}{5}\frac{\dot{U}_2}{4} + \frac{1}{6}\frac{\dot{U}_3}{5}} \\ &= \frac{\dot{U}_1}{\frac{\dot{U}_1}{5^2 \times 4} + \frac{\dot{U}_1}{6^2 \times 5}} = \frac{1}{\frac{1}{5^2 \times 4} + \frac{1}{6^2 \times 5}} \end{aligned}$$